


1] \Rightarrow Y connection laws:-

$\rightarrow * N_{ab} = V_{ao} + V_{ob}$

$\rightarrow * V_{ab} = 2 V_{phase}$

$\rightarrow * V_L = 2 V_{phase} \cos 30 = \sqrt{3} V_{phase}$

$\rightarrow * I_L = I_{phase}$

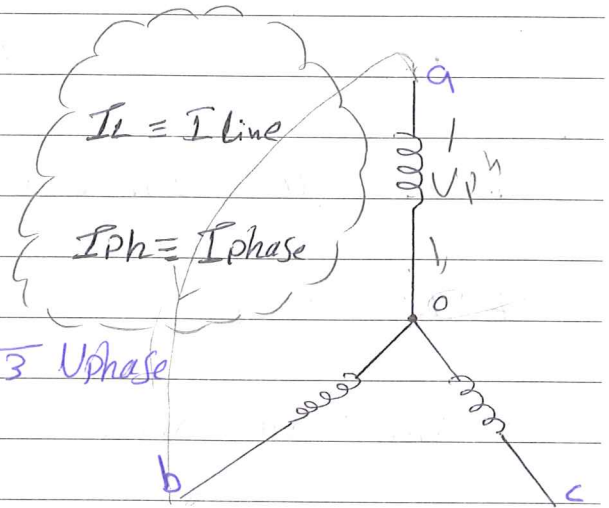

$\rightarrow * P.f = \cos \theta = \frac{R}{Z} = \frac{P}{S} = 1$

$\rightarrow * P_{ph} = V_{ph} \cdot I_{ph} = 3 \frac{V_L}{\sqrt{3}} \cdot I_L = \sqrt{3} V_L I_L$

$\rightarrow * P_T = 3 V_{ph} \cdot I_{ph}$




* When power factor < 1

$P \Rightarrow \text{"True power"} = \sqrt{3} V_L I_L \cos \phi$

$Q \Rightarrow \text{"Reactive power"} = \sqrt{3} V_L I_L \sin \phi$

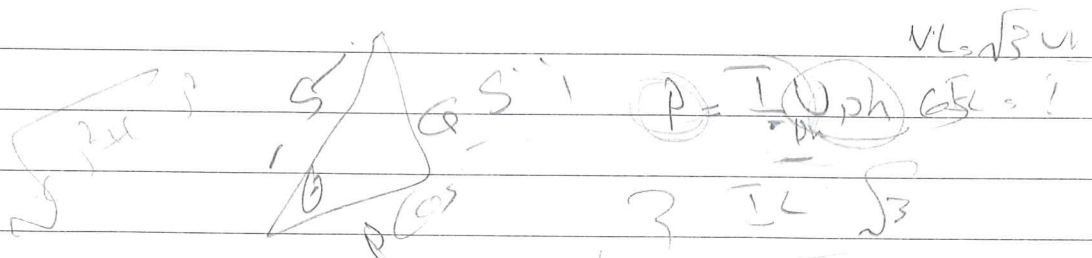$S \Rightarrow \text{"Apparent power"} = P + jQ = \sqrt{3} V_L I_L$



Date:

No.



[2] Delta Connection Laws :-

1) When power factor = 1


$$* I_a = I_L = I_{ab} + I_{ac}$$

$$* I_L = 2 I_{ph} \cos 30^\circ = \sqrt{3} I_{ph}$$

$$* V_{ab} = V_L = V_{ph}$$

$$* P_{ph} = V_{ph} \cdot I_{ph}$$
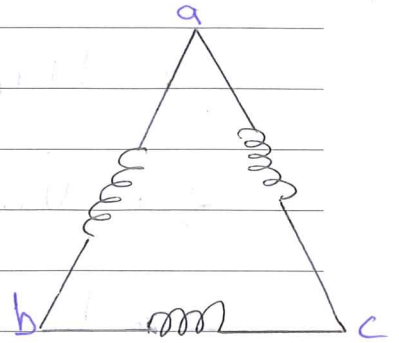
$$* P_T = 3 V_L \cdot \frac{I_L}{\sqrt{3}} = \sqrt{3} V_L I_L$$



2) When $pf < 1$

$$* P = \sqrt{3} V_L I_L \cos \theta$$


$$* Q = \sqrt{3} V_L I_L \sin \theta$$

$$* S = \sqrt{3} V_L I_L$$

Date:

No.

* Star to Star with a neutral wire:-

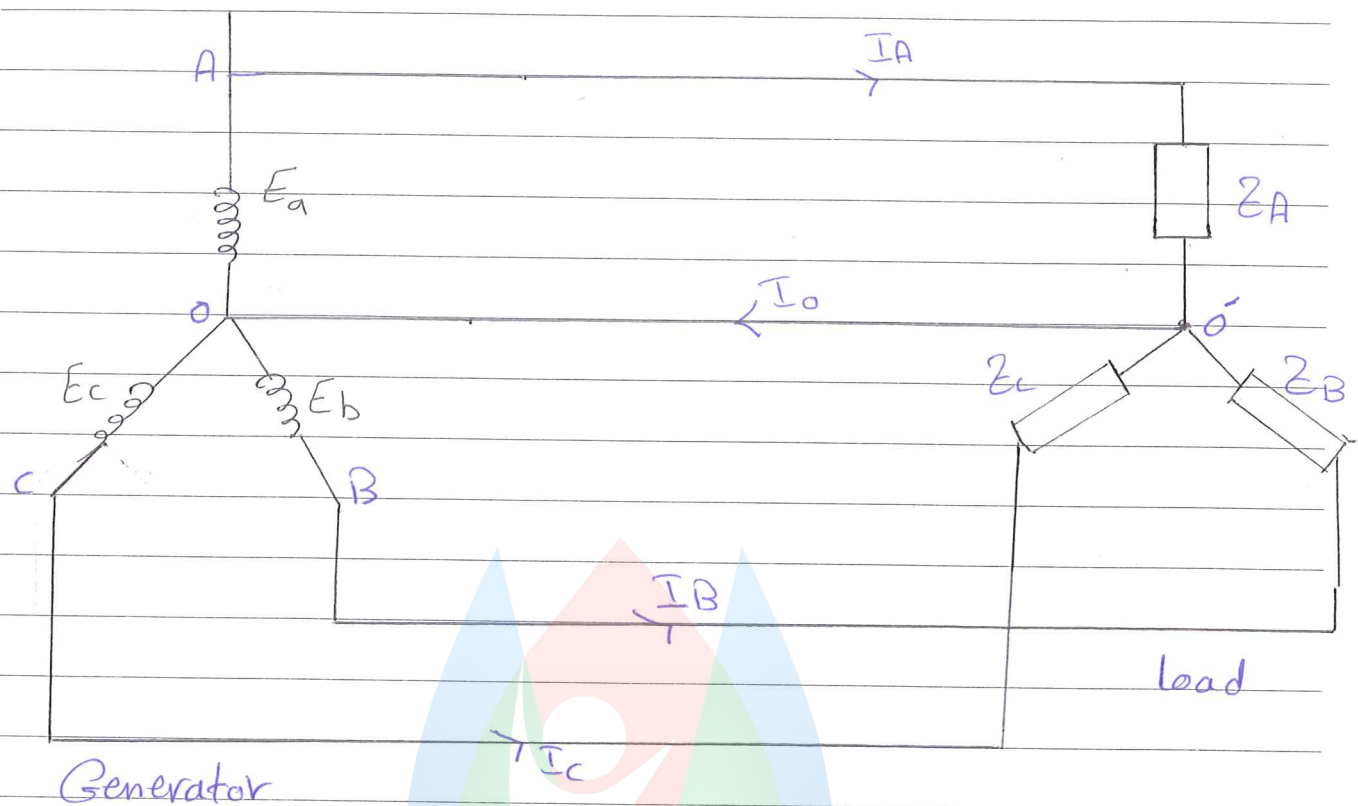

* If Z_A, Z_B, Z_C is very small "low" then the potential at o' practically the same as the potential at o

$$I_A = \frac{E_A}{Z_A}, \quad I_B = \frac{E_B}{Z_B}, \quad I_C = \frac{E_C}{Z_C}$$

By applying KCL $I_o = I_A + I_B + I_C$


If $Z_A = Z_B = Z_C \Rightarrow$ load is Balanced

then $I_o = \text{zero}$

If load isn't Balanced $I_o \neq \text{zero}$



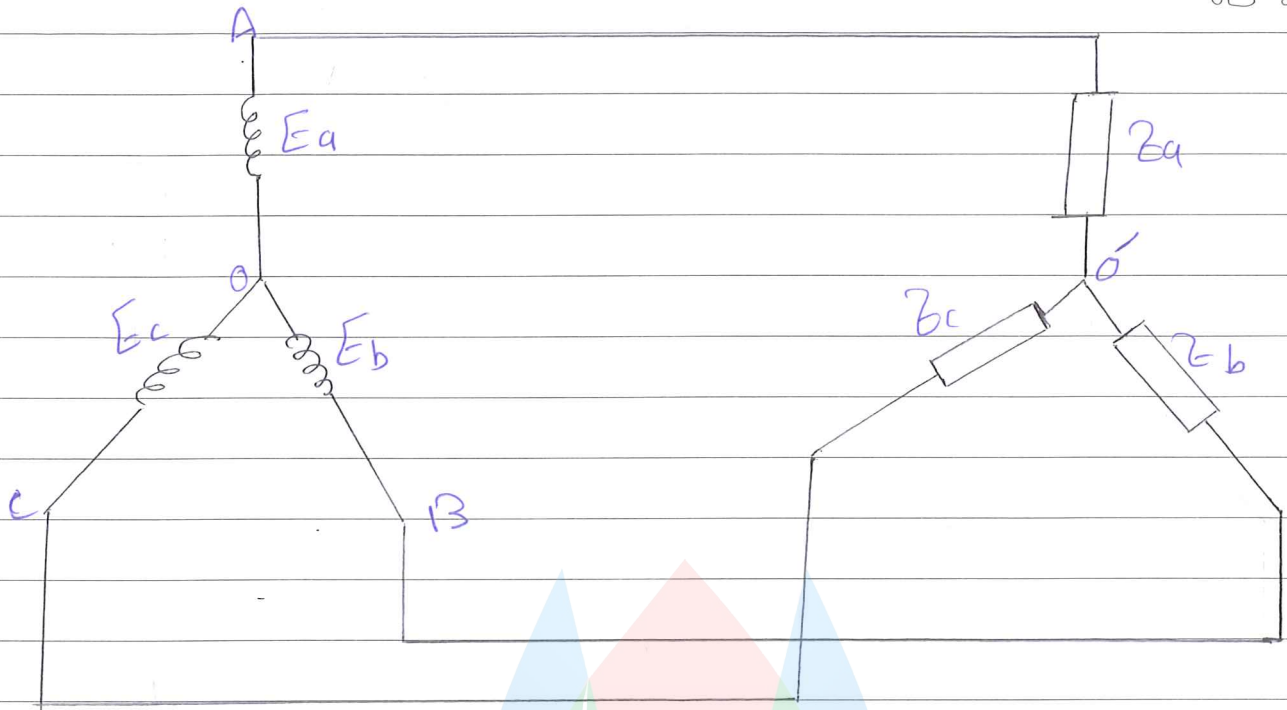* Star to Star Connection without a Neutral Wire:



$$V_{O'O} = \frac{E_A Y_A + E_B Y_B + E_C Y_C}{Y_A + Y_B + Y_C} \quad \text{where } Y_A, Y_B, Y_C \text{ are admittances}$$

With Balanced Loads:- $Y_A = Y_B = Y_C$

$$\therefore V_{O'O} = \frac{Y_A (E_A + E_B + E_C)}{3 Y_A} = \frac{1}{3} (E_A + E_B + E_C) = 0$$

$$V_{AO'} = E_A \quad \text{and} \quad V_{BO'} = E_B \quad \text{and} \quad V_{CO'} = E_C$$

\Rightarrow With unbalanced load:- $V_{O'O} \neq \text{Zero}$

$$\therefore V_{AO'} = E_A + V_{O'O}$$

$$V_{BO'} = E_B + V_{O'O}$$

$$V_{CO'} = E_C + V_{O'O}$$

Date:


No.

* phase current at the load end:-

$$I_a = \frac{V_{ao'}}{Z_A} \quad , \quad I_b = \frac{V_{bo'}}{Z_b} \quad , \quad I_c = \frac{V_{co'}}{Z_c}$$



[12] Star-Delta Connection :-

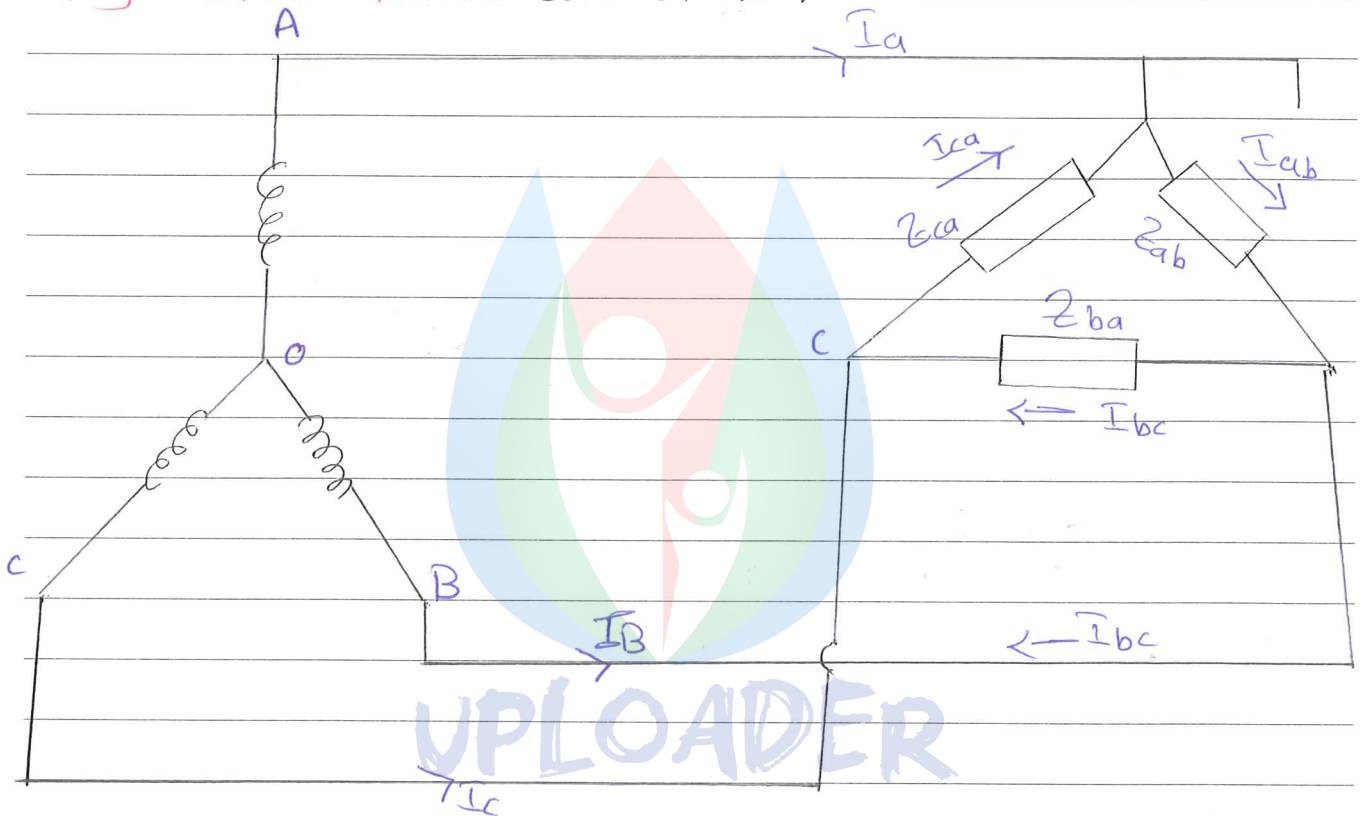

$$* I_A = I_{ab} - I_{ca} \quad , \quad I_B = I_{bc} - I_{ab}$$

$$I_c = I_{ca} - I_{bc} \quad \text{if the load is balanced}$$

the line current is $I_L = \sqrt{3} I_{ph}$